

Keywords: programmable gain amplifier, PGA, MAX532, programmable gain, programmable resistor, ac gain control

APPLICATION NOTE 429

Programmable-Gain Amplifier, Using the MAX532 DAC

Nov 01, 2000

Abstract: This application note discusses how to use the MAX532 to build a programmable gain amplifier (PGA) that's suitable for AC gain control. No external components are necessary. Equations are provided to easily calculate the output values.

The MAX532 is a dual, 12-bit, voltage-output DAC. Access to the output amplifier's input terminals allows it to be easily configured as a programmable-gain amplifier (PGA) suitable for AC gain control.

The circuit configuration is that of an inverting amplifier, with R2 replaced by the effective resistance of the DAC ladder (**Figure 1**) and R1 replaced by internal feedback resistor RFB (**Figure 2**). In this circuit, an AC signal is applied to the feedback resistor input and the output signal is tied to the DAC reference input. The maximum signal at VOUT is limited by the amplifier's headroom from the supply rails ($\pm 12V$ to $\pm 15V$), which must be a minimum of 2.5V from either rail.

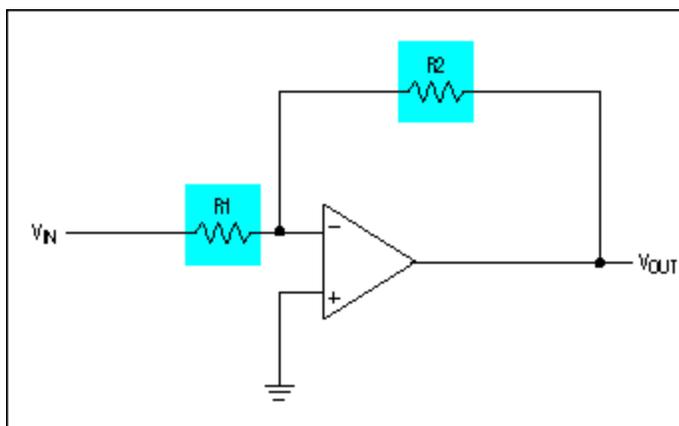


Figure 1. Fixed-gain inverting amplifier.

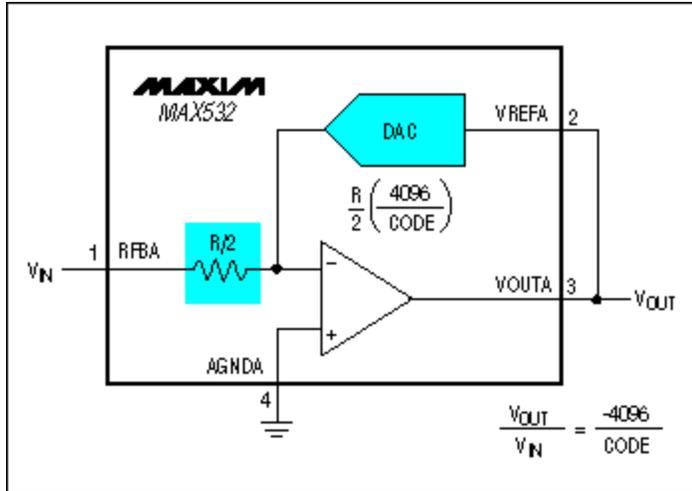


Figure 2. Programmable-gain amplifier.

The DAC functions as a programmable resistor in the feedback of the amplifier such that :

$$V_{OUT}/V_{IN} = -R(DAC)/R_{FB},$$

where R(DAC) is the resistance of the DAC ladder and RFB is the value of the feedback resistor, which is R/2.

$R(DAC) = R/2 \times [4096 / (DAC \text{ CODE})]$, with the DAC CODE given as a decimal value. As the code decreases, the effective DAC resistance increases, and so the gain increases. The transfer function for the circuit is thus:

$$\frac{V_{OUT}}{V_{IN}} = \frac{-4096}{DAC \text{ CODE}}$$

The code can be programmed between 1 and full scale ($2^{12}-1$). Zero code is not allowed, as it results in the DAC's appearing as an open circuit in the feedback loop.

Related Parts

[MAX532](#)

Dual, Serial Input, Voltage-Output, Multiplying, 12-Bit DAC

[Free Samples](#)

More Information

For Technical Support: <http://www.maximintegrated.com/support>

For Samples: <http://www.maximintegrated.com/samples>

Other Questions and Comments: <http://www.maximintegrated.com/contact>

Application Note 429: <http://www.maximintegrated.com/an429>

APPLICATION NOTE 429, AN429, AN 429, APP429, Appnote429, Appnote 429

Copyright © by Maxim Integrated Products

Additional Legal Notices: <http://www.maximintegrated.com/legal>